

Assignment Problem: Combinational (ALU OP)circuit using Verilog

Category: A,B,C

Word Size = 6

ALU Operations = XOR AND OR ((A xor B) and (A or B)),SHR

Solution:

[Github repo](#)

Video:

Have you uploaded the video?	YES
Check List 1: Have you explained the design using testbenches to prove that your circuit is working correctly and giving correct results?	YES
Check List 2: Have you shown full synthesis results showing all the required info including RTL Synthesis, RTL Floorplan, RTL Power Analysis, GDS and Heatmap (for details, see assignment template doc)?	YES

HDL Code:

Check List: Have you added all the modules written in verilog including ALU, ALU_OP1, ALU_OP2, CONTROLLER, TOP, TOP_TESTBENCH, ALU_TESTBENCH, CONTROLLER_TESTBENCH?	YES
--	-----

ALU

```
module ALU (
    input wire [5:0] A, B,           // 6-bit inputs A and B
    input wire OP,                   // 1-bit operation code
    output reg [5:0] R,               // 6-bit result
    output wire CF,                   // Carry flag
    output wire SF,                   // Sign flag
    output wire ZF,                   // Zero flag
);

    wire [5:0] R_XANDOR;              // Result from XANDOR module
    wire [5:0] R_SHR;                 // Result from SHR module

    // Instantiate modules
    ALU_XOR_AND_OR_6bit XANDOR1 (
        .A(A),
        .B(B),
        .result(R_XANDOR)
    )
endmodule
```

```

);

ALU_SHR_6bit SHR1 (
    .in(A),
    .shift(B[2:0]),
    .out(R_SHR)
);

// Operation selection
always @(*) begin
    case (OP)
        1'b0: begin
            R = R_XANDOR; // XANDOR
        end
        1'b1: begin
            R = R_SHR; // SHR
        end
        default: begin
            R = 6'b000000; // Default case
        end
    endcase
end

// Flag assignments
assign CF = 1'b0; // No carry for XANDOR or SHR
assign SF = R[5]; // Sign flag: MSB of result
assign ZF = ~(R[5] | R[4] | R[3] | R[2] | R[1] | R[0]); // Zero
flag: NOR of result bits

endmodule

```

ALU_OP1

```

module ALU_XOR_AND_OR_6bit(
    input wire [5:0]A, //6 bit input A
    input wire [5:0]B, //6 bit input B
    output wire [5:0]result//6 bit result
);
    assign result= (A^B) & (A|B);
endmodule

```

ALU_OP2

```
module ALU_SHR_6bit (  
    input wire [5:0] in,          // 6-bit input  
    input wire [2:0] shift,      // 3-bit input shift  
    output reg [5:0] out // 6-bit output  
);  
  
    always @(*) begin  
        case (shift)  
            3'b000: out = in;                // No shift  
            3'b001: out = {1'b0, in[5:1]};   // Right shift by 1 bit  
            3'b010: out = {2'b00, in[5:2]};   // Right shift by 2 bits  
            3'b011: out = {3'b000, in[5:3]};   // Right shift by 3 bits  
            3'b100: out = {4'b0000, in[5:4]};   // Right shift by 4 bits  
            3'b101: out = {5'b00000, in[5]};   // Right shift by 5 bits  
            3'b110: out = 6'b000000;           // Right shift by 6 bits  
(all zeros)  
            3'b111: out = 6'b000000;           // Right shift by 7 bits  
(all zeros)  
        endcase  
    end  
endmodule
```

TOP

```
module top
(
    input wire clk,reset,
    output wire [5:0]result,
    output wire flag_zero
);

wire [5:0]A,B;
wire OP;
wire [5:0] R_result;

controller controller1(
    .clk(clk) ,
    .reset(reset) ,
    .A(A) ,
    .B(B) ,
    .OP(OP)
);

ALU datapath1(
    .A(A) ,
    .B(B) ,
    .OP(OP) ,
    .result(R_result) ,
    .ZF(R_ZF)
);

assign result=R_result;
assign flag_zero=~R_ZF;

endmodule
```

CONTROLLER

```
module controller(  
    input wire clk,reset,  
    output reg [5:0]A,B,  
    output reg OP  
);  
reg [2:0]pstate,nstate;  
parameter[2:0]START= 3'b000, //state  
    ONE= 3'b001,  
    TWO= 3'b010,  
    THREE=3'b011,  
    FINISH=3'b100;  
//state Register  
always @(posedge clk or posedge reset)  
begin  
    if(reset)  
        pstate <= START;  
    else  
        pstate <= nstate;  
end  
//Next state and Outputs  
always @(*) begin  
    A=6'b000000;  
    B=6'b000000;  
    OP=1'b0;  
    nstate=pstate;  
  
    case (pstate)  
    START:  
    begin  
        nstate = ONE;  
    end  
    ONE:  
    begin  
  
    end  
    TWO:  
    begin  
  
    end  
    end  
end
```

```

    THREE:
    begin
        nstate = FINISH;
    end

    FINISH:
    begin
        nstate = FINISH;
    end

    default
    : begin
        nstate = START;
    end

    endcase
end

// Output logic
always @(*) begin
    case (pstate)
        ONE: begin
            A = 6'b101010; // Example values
            B = 6'b010101;
            OP = 1'b0; //XOR AND OR
            nstate = TWO;
        end
        TWO: begin
            A = 6'b111100;
            B = 6'b000011;
            OP = 1'b0; //XOR AND OR
            nstate = THREE;
        end
        THREE: begin
            A = 6'b100001; // SHR
            B = 6'b000000;
            OP = 1'b1; //
            nstate=FINISH;
        end
        FINISH: begin
            nstate=START;
        end
        default:nstate=START;
    endcase
end
endmodule

```

Top Testbench

```
`timescale 1ns/1ns
module top_tb;
reg clk,reset;
wire [5:0]result;
wire flag_zero;
top uut(
    .clk(clk),
    .reset(reset),
    .result(result),
    .flag_zero(flag_zero)
);
initial begin
    clk=0;
    forever #5 clk=~clk
end

initial begin
    $dumpfile("top_test.vcd");
    $dumpvars(0,top_tb);
    reset=1;    #10
    reset=0;    #15
    reset=1;    #20
    reset=0;    #100
    $finish
end
endmodule
```

Controller_Testbench

```
`timescale 1ns/1ns
module controller_tb;
reg clk, reset;
wire [5:0] A, B;
wire OP;

controller uut(
    .clk(clk),
    .reset(reset),
    .A(A),
    .B(B),
    .OP(OP)
);

initial begin
    clk = 0;
    forever #5 clk = ~clk;
end

initial begin
    $dumpfile("Controller_test.vcd");
    $dumpvars(0, controller_tb);
    reset = 1;    #10;
    reset = 0;    #100;
    $finish;
end

endmodule
```

ALU_Testbench

```
`timescale 1ns / 1ps

module ALU_tb;

    // Signals for ALU
    reg [5:0] A, B;           // ALU inputs
    reg OP;                   // ALU operation code (1-bit)
    wire [5:0] R;             // ALU output
    wire CF;                  // Carry flag
    wire SF;                  // Sign flag
    wire ZF;                  // Zero flag

endmodule
```



```

// Instantiate ALU module
ALU uut (
    .A(A) ,
    .B(B) ,
    .OP(OP) ,
    .R(R) ,
    .CF(CF) ,
    .SF(SF) ,
    .ZF(ZF)
);

// Dump file setup and test procedure
initial begin
    $dumpfile("alu_test.vcd"); // Output VCD file
    $dumpvars(0, ALU_tb);      // Dump all variables in the testbench

    // Initialize inputs
    A = 6'b000000;
    B = 6'b000000;
    OP = 1'b0;

    // Test XANDOR operation (OP = 0)
    $display("\nTesting XOR AND OR Operation ((A XOR B) AND (A OR
B)):");
    A = 6'b101010; B = 6'b010101; OP = 1'b0; // Test case 1
    #10 $display("XOR AND OR: A=%b, B=%b, R=%b, SF=%b, ZF=%b", A, B,
R, SF, ZF);

    // Test SHR operation (OP = 1)
    $display("\nTesting SHR Operation (Right Shift):");
    A = 6'b101011; B = 3'b001; OP = 1'b1; // Shift by 1
    #10 $display("SHR by 1: A=%b, shift=%d, R=%b, SF=%b, ZF=%b", A,
B[2:0], R, SF, ZF);

    // Finish simulation
    #10 $finish;
end


endmodule

```

RTL Timing Diagram:

Check List: Have you added all the timing diagrams of ALU_TESTBENCH, CONTROLLER_TESTBENCH, TOP_TESTBENCH?	NO Only ALU_TEST BENCH
--	---------------------------------

Alu_tb.v

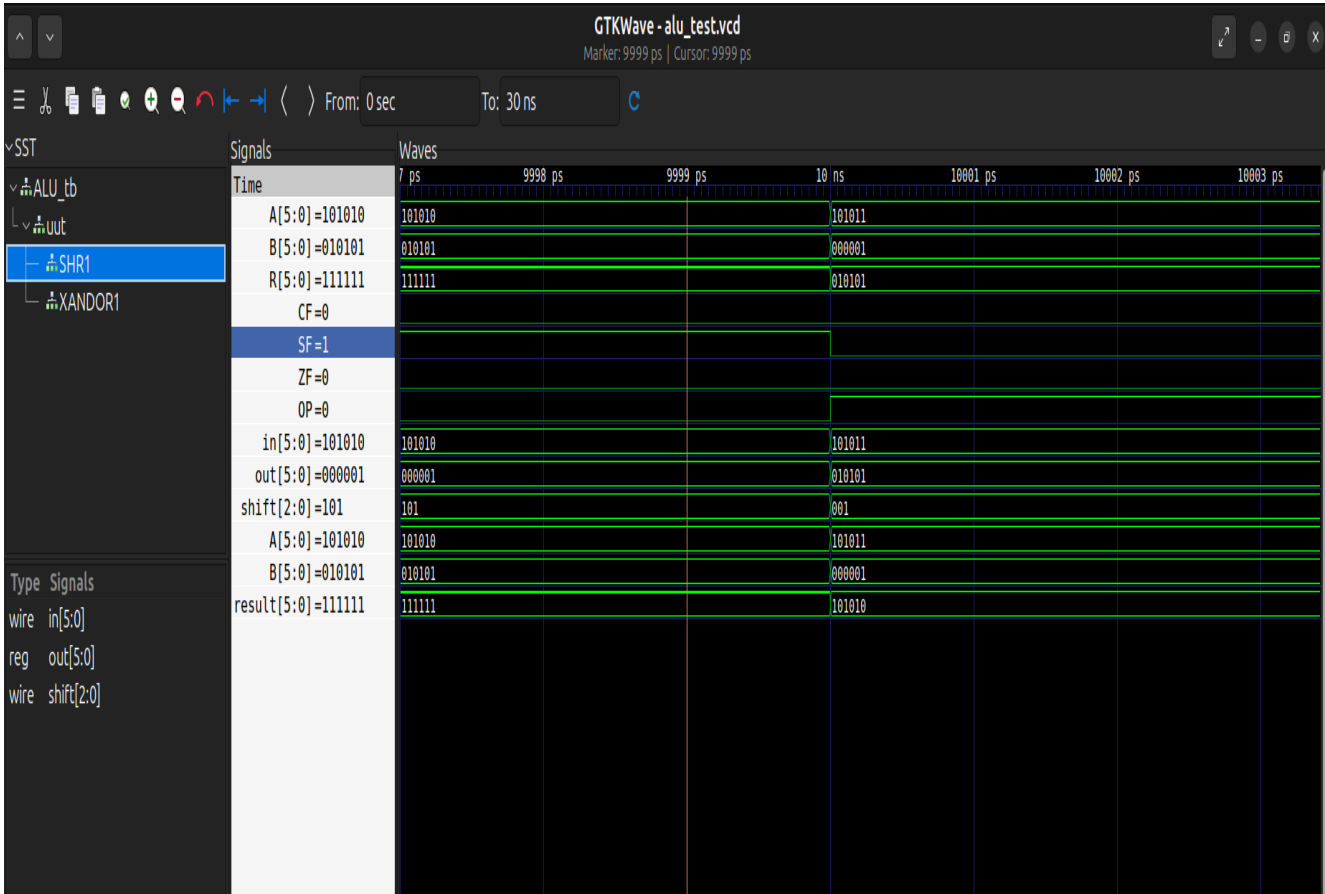

Controller

```
raesalghul@raesalghul: ~/Downloads/circuit-assignment/circuit-assignment
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ ls
alu_op.vvp      ALU.v      controller_test.vvp  top_tb.v
ALU_SHR_6bit.v  ALU_XOR_AND_OR_6bit.v  controller.v      top.v
ALU_tb.v        controller_tb.v      MAKEFILE
alu_test.vcd    Controller_test.vcd  README.md
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ iverilog -o controller_test.vvp controller_tb.v controller.v
controller_tb.v:8: warning: Port 5 (OP) of controller expects 2 bits, got 1
controller_tb.v:8:      : Padding 1 high bits of the port.
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ vvp controller_test.vvp
VCD info: dumpfile Controller_test.vcd opened for output.
controller_tb.v:33: $finish called at 100 (1ns)
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ gtwave Controller_test.vcd

GTKWave Analyzer v3.3.116 (w)1999-2023 BSI

Error opening .vcd file 'controller_test.vcd'.
Why: No such file or directory
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$
```

Top

```
symbol: __libc_pthread_init, version GLIBC_PRIVATE
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ iverilog -o top_test.vvp top_tb.v top.v controller.v ALU.v ALU_XOR_AND_OR_6bit.v ALU_SHR_6bit.v
top.v:4: syntax error
top.v:1: Errors in port declarations.
controller.v:1: error: Module definition controller cannot nest into module controller.
ALU.v:1: error: Module definition ALU cannot nest into module controller.
ALU_XOR_AND_OR_6bit.v:1: error: Module definition ALU_XOR_AND_OR_6bit cannot nest into module controller.
ALU_SHR_6bit.v:1: error: Module definition ALU_SHR_6bit cannot nest into module controller.
ALU_SHR_6bit.v:22: syntax error
I give up.
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ vvp top_test.vvp
top_test.vvp: Unable to open input file.
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$ gtwave top_test.vcd
gtkwave: symbol lookup error: /snap/core20/current/lib/x86_64-linux-gnu/libpthread.so.0: undefined symbol: __libc_pthread_init, version GLIBC_PRIVATE
raesalghul@raesalghul:~/Downloads/circuit-assignment/circuit-assignment$
```

RTL Synthesis (130nm Skywater PDK with OpenLane toolchain):

Check List: Have you added *RTL synthesis summary*, *RTL synthesized design figure* and *Standard cell usage in synthesized design*?


YES

RTL synthesis summary

```
1 110. Printing statistics.
2
3 === ALU ===
4
5     Number of wires:          48
6     Number of wire bits:      63
7     Number of public wires:    7
8     Number of public wire bits: 22
9     Number of ports:          7
10    Number of port bits:       22
11    Number of memories:        0
12    Number of memory bits:     0
13    Number of processes:       0
14    Number of cells:           50
```

RTL synthesized design figure (Following figure is showing what info need to be shown /Just copy paste these figures)

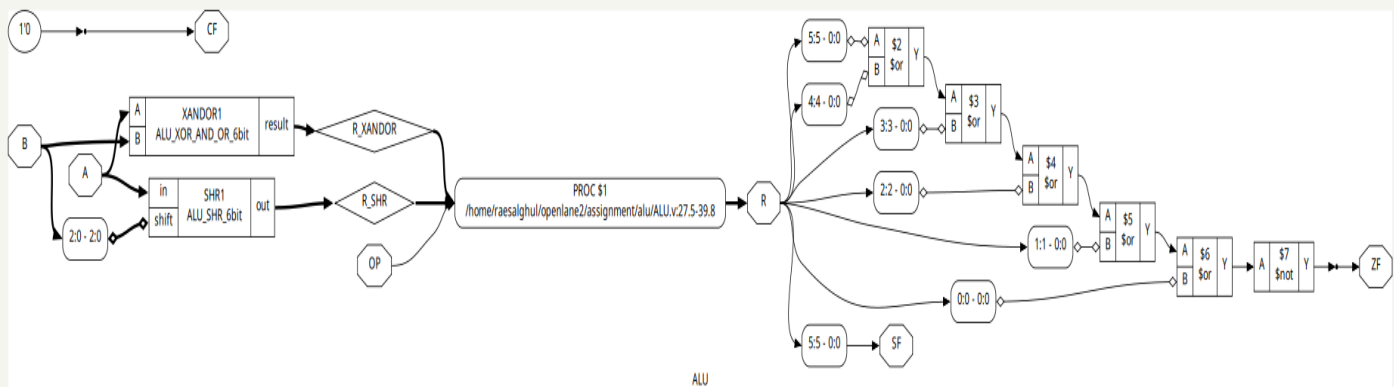There will be 2 figures in 2 .dot files in the synthesis folder. Show them both.



Standard cell usage in synthesized design (Following table is showing what info need to be shown /Just copy paste these info from terminal here)

15	sky130_fd_sc_hd__a21bo_2	2
16	sky130_fd_sc_hd__a22oi_2	1
17	sky130_fd_sc_hd__a31o_2	2
18	sky130_fd_sc_hd__a32o_2	3
19	sky130_fd_sc_hd__a41o_2	1
20	sky130_fd_sc_hd__and2b_2	2
21	sky130_fd_sc_hd__and3_2	2
22	sky130_fd_sc_hd__and4_2	1
23	sky130_fd_sc_hd__and4b_2	1
24	sky130_fd_sc_hd__and4bb_2	2
25	sky130_fd_sc_hd__buf_2	1
26	sky130_fd_sc_hd__conb_1	1
27	sky130_fd_sc_hd__inv_2	4
28	sky130_fd_sc_hd__mux2_1	1
29	sky130_fd_sc_hd__nand2_2	2
30	sky130_fd_sc_hd__nor2_2	1
31	sky130_fd_sc_hd__nor3_2	2
32	sky130_fd_sc_hd__nor4_2	1
33	sky130_fd_sc_hd__o21ai_2	2
34	sky130_fd_sc_hd__o21ba_2	3
35	sky130_fd_sc_hd__o22a_2	3
36	sky130_fd_sc_hd__o31a_2	1
37	sky130_fd_sc_hd__or2_2	4
38	sky130_fd_sc_hd__or3_2	4
39	sky130_fd_sc_hd__xor2_2	3
40		

RTL Floorplan (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added RTL Floorplan info?	YES
--	-----

(Following table is showing what info need to be shown /Just copy paste these info from terminal here)

```
[INFO] [11-0030] Inserted 0 cells using sky130_fd_sc_hd__cond_1/n1.
[INFO] Extracting DIE_AREA and CORE_AREA from the floorplan
[INFO] Floorplanned on a die area of 0.0 0.0 50.0 50.0 (µm).
[INFO] Floorplanned on a core area of 5.52 10.88 44.16 38.08 (µm).
Writing metric design__die__bbox: 0.0 0.0 50.0 50.0
Writing metric design__core__bbox: 5.52 10.88 44.16 38.08
Setting global connections for newly added cells...
[INFO] Setting global connections...
Updating metrics...
Cell type report: Count Area
```

RTL Power Analysis (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added RTL Power Analysis info?	YES
---	-----

(Following table is showing what info need to be shown /Just copy paste these info from terminal here)

Open power.rpt Save

~/openlane2/assignment/alu/runs/RUN_2025-06-1...47-11/54-openroad-stapostpnr...


```
1 |
2 |=====
3 | report_power
4 |=====
5 |===== nom_tt_025C_1v80 Corner =====
6 |
7 | Group           Internal   Switching   Leakage     Total
8 |                   Power      Power      Power      Power (Watts)
9 |-----
10| Sequential      0.000000e+00 0.000000e+00 0.000000e+00 0.000000e+00 0.0%
11| Combinational   1.080277e-05 1.700216e-05 2.737968e-10 2.780520e-05 100.0%
12| Clock           0.000000e+00 0.000000e+00 1.522820e-10 1.522820e-10 0.0%
13| Macro           0.000000e+00 0.000000e+00 0.000000e+00 0.000000e+00 0.0%
14| Pad             0.000000e+00 0.000000e+00 0.000000e+00 0.000000e+00 0.0%
15|-----
16| Total           1.080277e-05 1.700216e-05 4.260789e-10 2.780535e-05 100.0%
17|                 38.9%      61.1%      0.0%
18|
```


GDS Layout (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added the GDS Layout figure?

YES/NO

 (Following figure is showing what info need to be shown /Just copy paste these figures)



Heatmap (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added the heatmap?

YES

NB: Failing to add any required info will cause point penalty (1-2 Marks)

